

Lab4_有限状态机

金泽文 pb15111604

实验目的：

- 进一步学习时序逻辑电路
- 了解有限状态机的工作原理
- 学会使用“三段式”有限状态机设计电路
- 掌握按键去抖动、信号取边沿等处理技巧

实验内容：

- 用三段式有限状态机实现序列检测功能电路
 - 按从高位到低位逐位串行输入一个序列
 - 每当检测到序列“1101”（不重叠）时，LED 指示灯亮，否则灭，例如
 - 输入：1 1 0 1 1 0 1 1 0 1
 - 输出：0 0 0 1 0 0 0 0 0 1
 - 用拨动开关输入检测序列
 - 按键按下的瞬间将拨动开关状态锁存
 - 注意防抖动（按键按下瞬间可能会有多次的电平跳变）

具体实现：

用 FSM 模块实现状态机，共 5 个状态。

用 key_jitter 模块实现去抖动功能，(以保持 10ms 以上为有效)

用 Output 实现数码管显示

实验结果：

成功实现。

实验分析：

再次因为语法不清楚，以及阻塞与非阻塞赋值之间的不清楚浪费了很长的时间，下次不能因为这些基本概念的混淆而浪费实现了。

意见建议：

暂无

附录：

代码：

顶层模块

```
`timescale 1ns / 1ps
```

```
module top(
```

```
input          clk,
```

```
input          rst_n,
```

```
input          btn,
```

```
input          In,
```

```
output         led,
```

```
output [3:0]   sel,
```

```
output [7:0]   data
```

```
);
```

```
wire Op;
```

```
wire out;
```

```
key_jitter    u_key_jitter(  
    .clk      (clk),  
    .rst_n    (rst_n),  
    .btn      (btn),  
    .Op       (Op)  
);
```

```
FSM           u_FSM(  
    .clk      (clk),  
    .rst_n    (rst_n),  
    .In       (In),  
    .Op       (Op),  
    .led      (led)  
);
```

```
Output        u_Output(  
    .clk      (clk),  
    .rst_n    (rst_n),  
    .Op       (Op),
```

```
.In          (In),  
.sel         (sel),  
.data        (data)  
);
```

```
endmodule
```

消除抖动模块

```
`timescale 1ns / 1ps
```

```
module key_jitter(  
    input          clk,  
    input          rst_n,  
    input          btn,  
    output reg      Op  
);
```

```
    reg            Ol;
```

```
    reg [18:0] cnt;
```

```

initial Ol    = 0;
always@(posedge  clk or negedge rst_n)
begin
    if(~rst_n)
        cnt<=19'h0;
    else
        begin
            if(Ol  ==btn)
                cnt<=19'h0;
            else
                cnt<=cnt+ 19'h1;
            if(cnt ==19'h511_999)
                begin
                    Ol =  btn;
                    cnt<=19'h0;
                end
            end
        end
    end
end

```

```

always@(posedge  clk)
begin

```

```

        if((cnt == 19'h511_999) && (Ol == 1))
            Op <= 1;
        if(Op == 1)
            Op <= 0;
    end

```

endmodule、

状态机模块

```
`timescale 1ns / 1ps
```

```
module FSM(
```

```
    input    clk,
```

```
    input    rst_n,
```

```
    input    In,
```

```
    input    Op,
```

```
    output reg led
```

```
);
```

```
parameter  S0 = 0, S1 = 1, S2 = 2, S3 = 3, S4 = 4;
```

```
reg    [2:0]  next_state;
```

```
reg    [2:0]    curr_state;
```

```
initial next_state = S0;
```

```
always@(posedge clk or negedge rst_n)
```

```
begin
```

```
    if(~rst_n)
```

```
        curr_state  <=  S0;
```

```
    else    if(Op)
```

```
        curr_state  <=  next_state;
```

```
end
```

```
always@(*) begin
```

```
    case(curr_state)
```

```
        S0: if(In) next_state <= S1; else next_state <= S0;
```

```
        S1: if(In) next_state <= S2; else next_state <= S0;
```

```
        S2: if(In) next_state <= S2; else next_state <= S3;
```

```
        S3: if(In) next_state <= S4; else next_state <= S0;
```

```
        S4: if(In) next_state <= S1; else next_state <= S0;
```

```
        default: next_state <= S0;
```

```
    endcase
```

```
end
```

```

always@(posedge    clk or   negedge rst_n) begin
    if(~rst_n)
        led <= 0;
    else    if(Op) begin
        case(curr_state)
            S0: if(In) led <=  0; else led <= 0;
            S1: if(In) led <=  0; else led <= 0;
            S2: if(In) led <=  0; else led <= 0;
            S3: if(In) led <=  1; else led <= 0;
            S4: if(In) led <=  0; else led <= 0;
            default: led <=  0;
        endcase
    end
end

endmodule

```

数码管显示模块

```

module Output(
    input          clk,
    input          rst_n,
    input          Op,

```



```
input                In,  
output reg  [3:0]  sel,  
output reg  [7:0]  data  
    );
```

```
reg  [16:0] sel_ctrl;  
reg  [7:0]   data1;  
reg  [7:0]   data2;  
reg  [7:0]   data3;  
reg  [7:0]   data4;
```

```
initial  sel_ctrl  = 17'h0;  
initial  sel       = 4'b1110;  
initial  data      = 8'b1111_1111;  
initial  data1     = 8'b1111_1111;  
initial  data2     = 8'b1111_1111;  
initial  data3     = 8'b1111_1111;  
initial  data4     = 8'b1111_1111;
```

```
always@(posedge  clk)  
begin  
    if(sel_ctrl ==17'd100_000)
```

```

        sel_ctrl    <=17'd0;
    else
        sel_ctrl    <=sel_ctrl    + 17'h1;
    end

always@(posedge    clk)
begin
    if(sel_ctrl ==17'd25000)
        sel <=4'b1110;
    else    if(sel_ctrl ==17'd50000)
        sel <=4'b1101;
    else    if(sel_ctrl ==17'd75000)
        sel <=4'b1011;
    else    if(sel_ctrl ==17'd100_000)
        sel <=4'b0111;
    end

always@(posedge    clk or negedge rst_n)
begin
    if(~rst_n)
    begin
        data1    <=8'b1111_1111;
    end
end

```

```

        data2    <=8'b1111_1111;

        data3    <=8'b1111_1111;

        data4    <=8'b1111_1111;
    end
    else if(Op)
    begin
        data4 <=data3;
        data3 <=data2;
        data2 <=data1;
        if(In)
            data1 <=8'b1001_1111;
        else
            data1 <=8'b0000_0011;
        end
    end
end

```

```

always@(*)
begin
    if(sel == 4'b1110)
        data = data1;
    else if(sel == 4'b1101)
        data = data2;

```

```


else if(sel == 4'b1011)
    data = data3;
else
    data = data4;
end

endmodule


```


原理图：

top 模块


 


key_jitter 模块

 

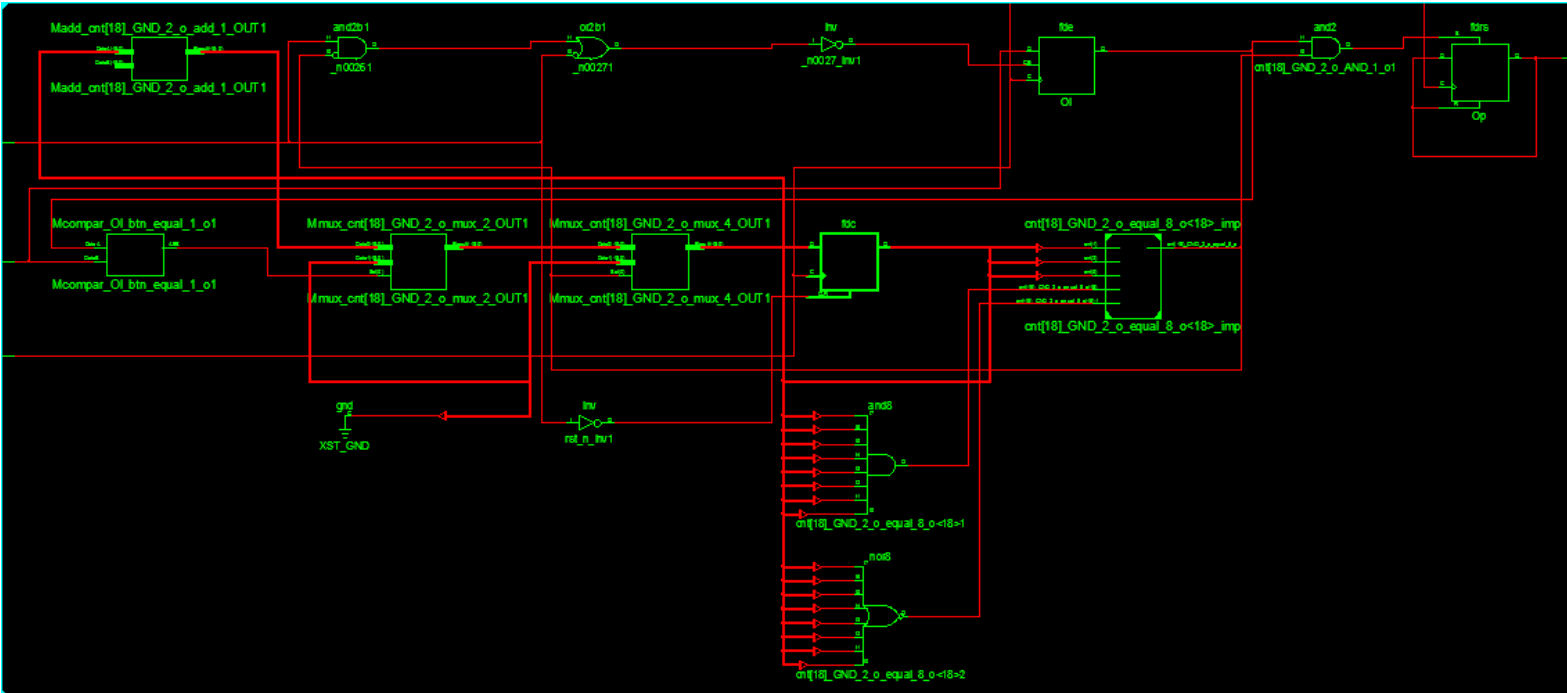

FSM 模块

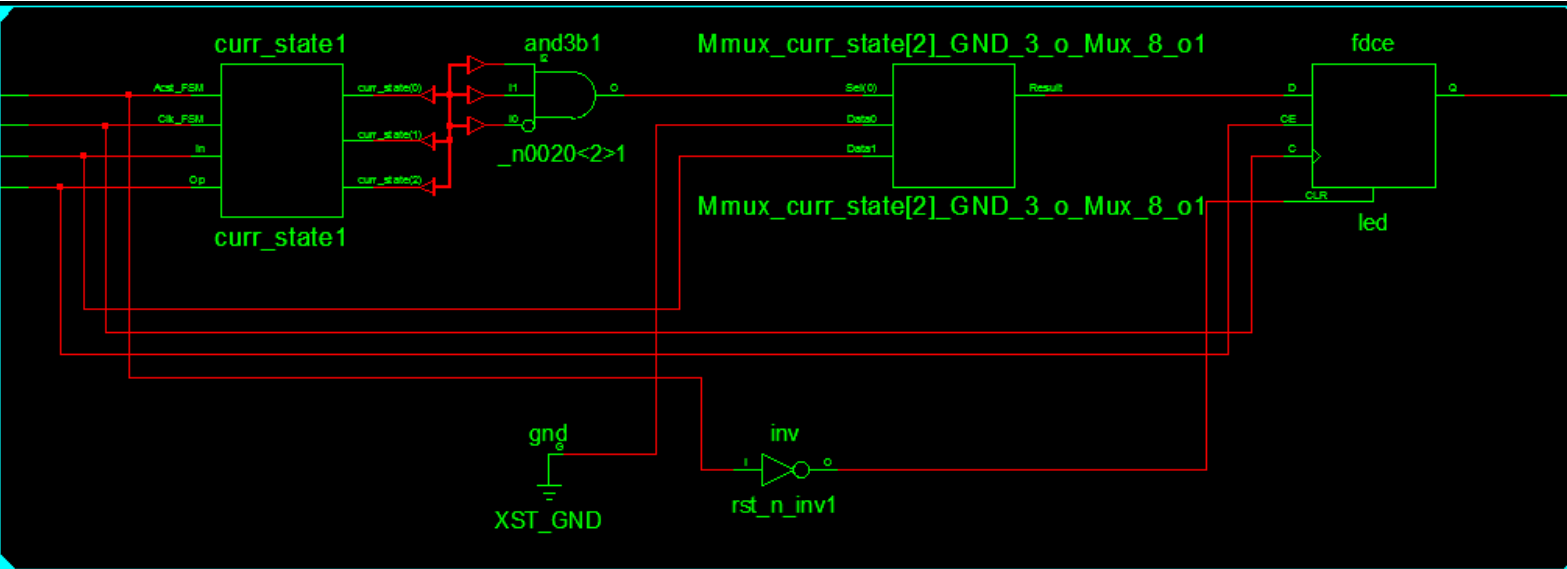 

u_FSM

Output 模块

