


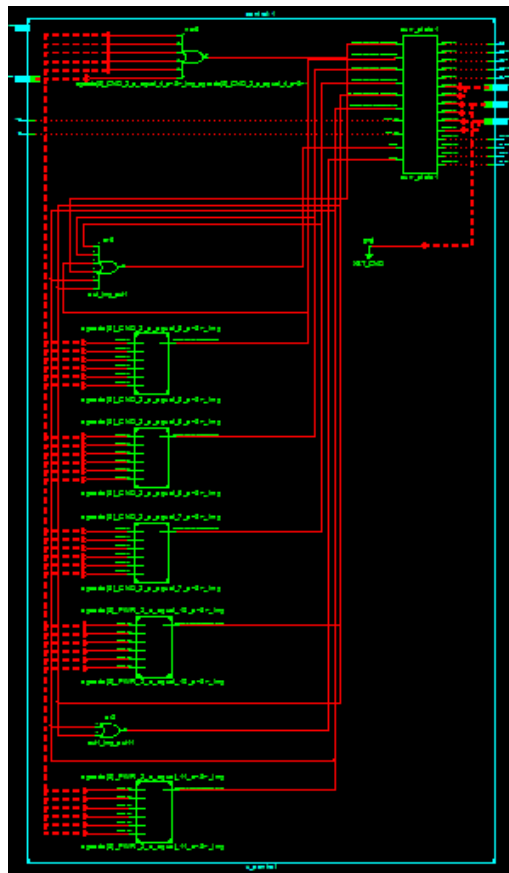




control 模块原理图:

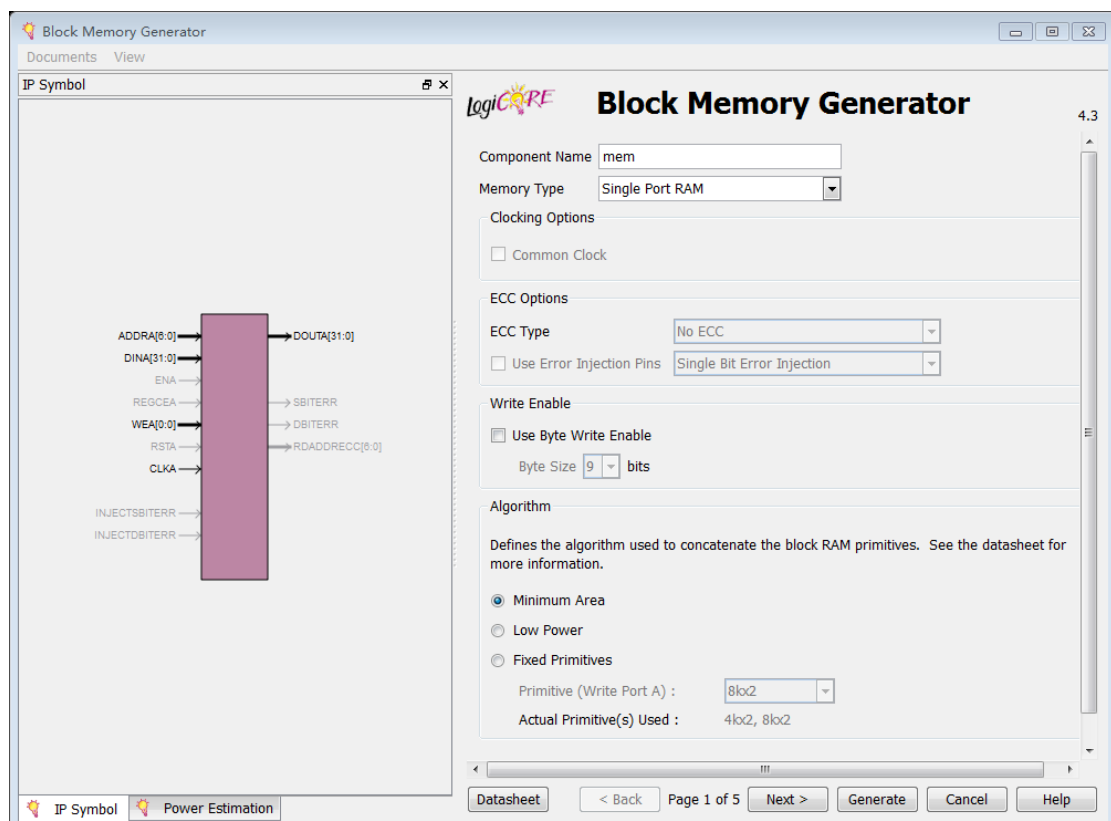

mem 初始化:

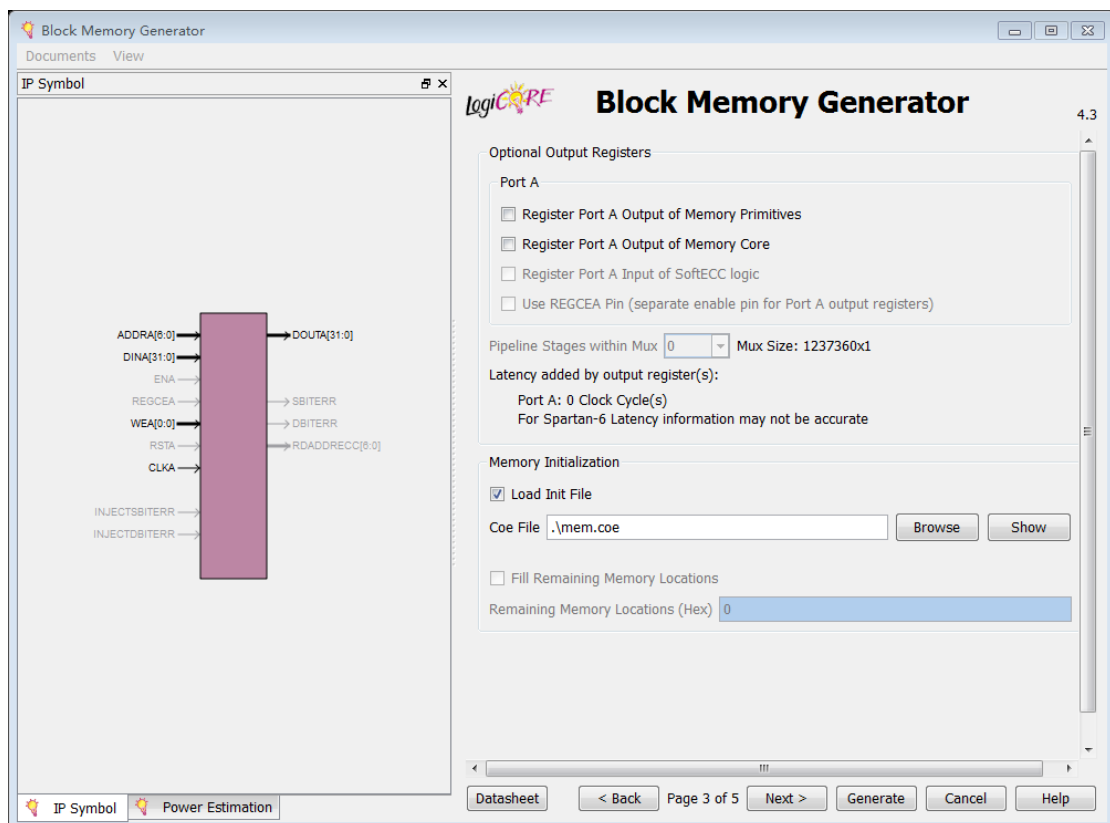

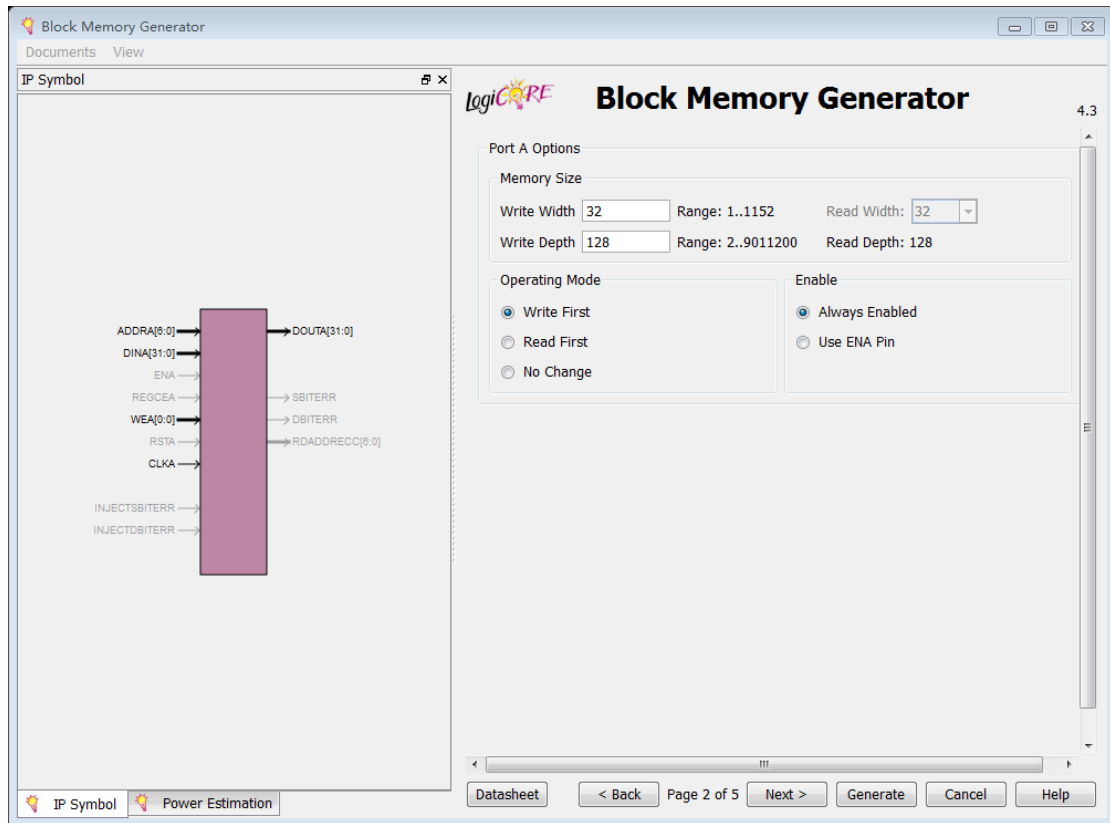

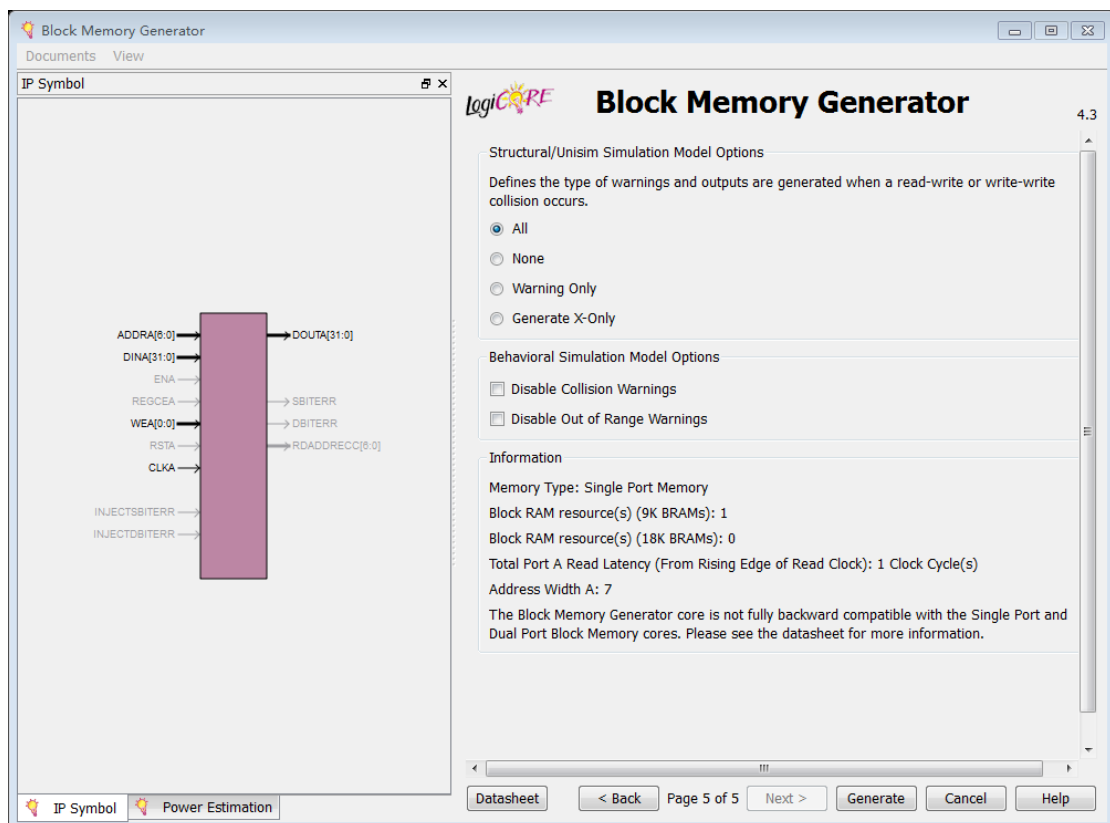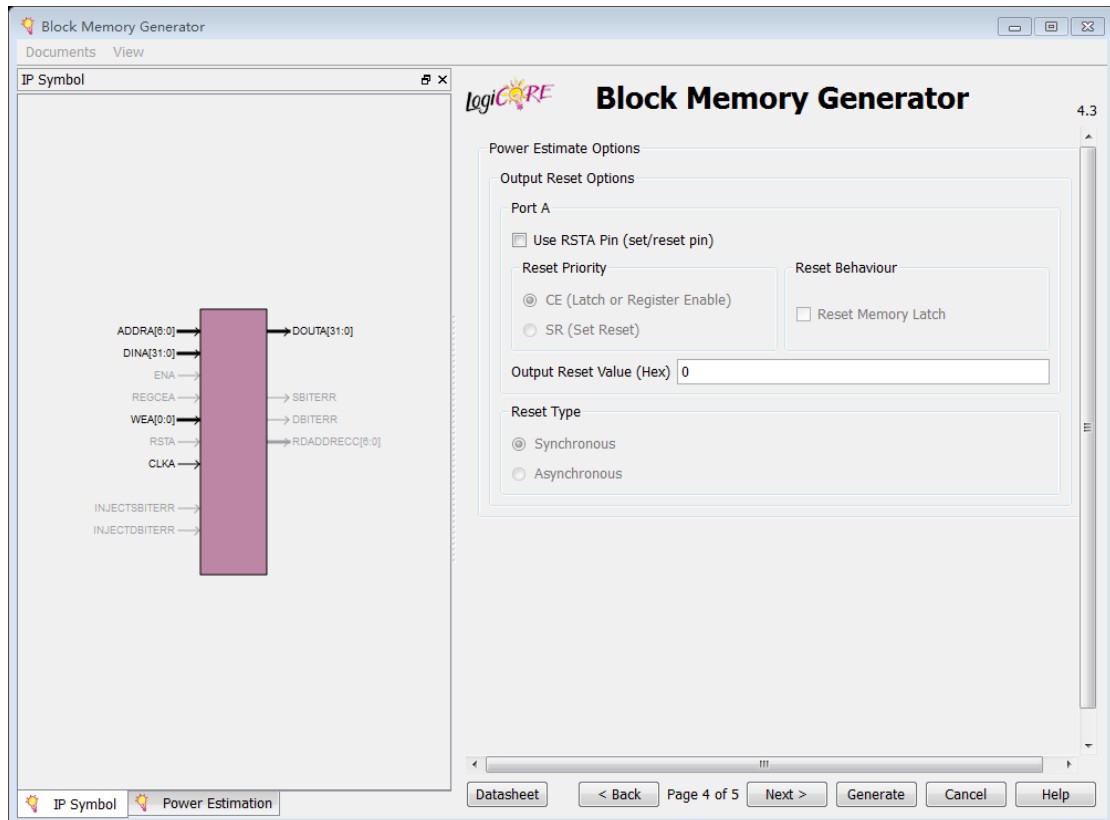

	0	1	2	3	4	5	6	7
0x0	20080100	200D0150	8DAD0000	200B0154	8D6B0000	200C0154	8D8C0004	AD0B0000
0x8	AD0C0004	21A9FFFE	8D0B0000	8D0C0004	016C5020	AD0A0008	21080004	2129FFFF
0x10	1D20FFF9	08000011	00000000	00000000	00000000	00000000	00000000	00000000
0x18	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x20	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x28	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x30	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x38	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x40	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x48	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x50	00000000	00000000	00000000	00000000	00000014	00000003	00000003	00000000
0x58	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x60	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x68	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x70	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
0x78	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

仿真结果:

mem 结果:

	0	1	2	3
0	3	3	6	9
4	15	24	39	63
8	102	165	267	432
12	699	1131	1830	2961
16	4791	7752	12543	20295
20	20	3	3	0

#### 四、实验分析


本实验无需下载，只需要进行仿真。

在 alu 模块中，首先输入两个带符号的 32 位（alu\_a 与 alu\_b）以及一个操作数（alu\_op），通过一个 case 语句将两个输入进行对应的运算，然后输出（alu\_out）。同时，在本实验中为了实现 bgtz 命令，外加一个 bgtz 接口，链接一组合逻辑电路，在 alu\_out 大于 0 时将 bgtz 置为 1，从而实现跳转功能。

在 REG\_FILE 模块中，按照提示的接口，先声明 32\*32 大小的空间存放数据，然后使用三个 always，第一个用于

写操作，当 r3\_wr 有效时将 r3\_addr 处的数据更改为 r3\_din；第二，三个用于对输出的赋值，分别将 r1\_addr, r2\_addr 处的数据输出到 r1\_dout, r2\_dout 处。

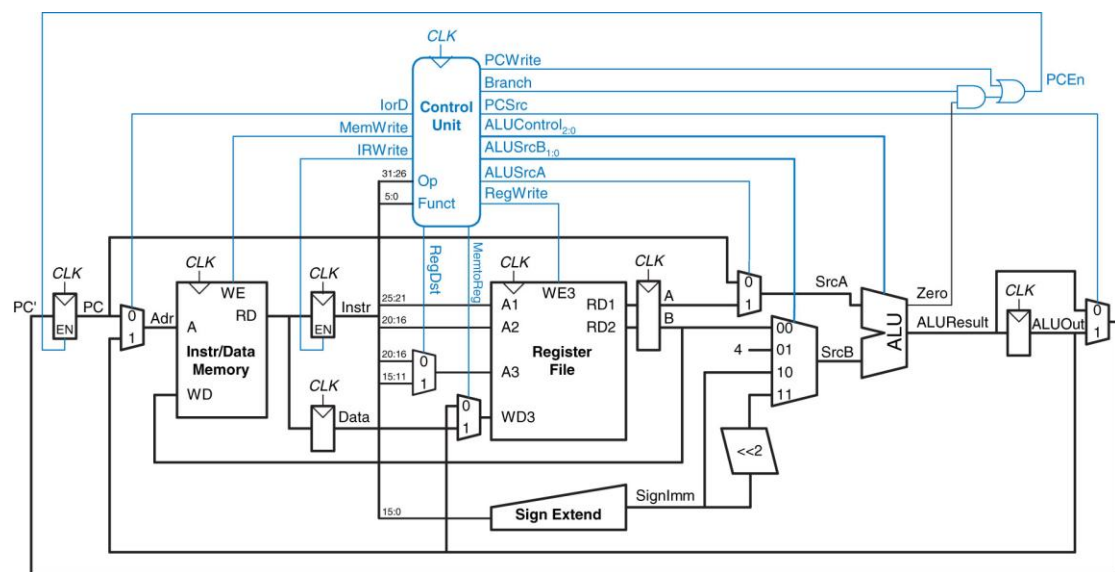在 control 模块中，设计一个简单的状态机，按照下图进行接口的连接，根据 op 和 funct 进行状态的转换，分别给多个输出赋值，以实现各个指令的功能。



**注意：此图片省略了 jump 电路，具体参考代码**


状态机如下图所示，在状态机的设计中，第一段对 rst\_n 进行判断，若有效则将当前状态初始化，否则根据 clk 的上升沿跳入下一个状态。第二段设计一组合逻辑电路根据输入与当前状态更改下一状态。第三段设计一个组合逻辑电路根据当前状态给各个输出变量赋值。值得注意的是，由于同步读取的时延关系在多个状态后添加了等待读取状态，其中包括：

3, 4 状态间 1 个等待周期。

5 状态后 2 个等待周期。

8 状态后 1 个等待周期。

11 状态后 1 个等待周期。

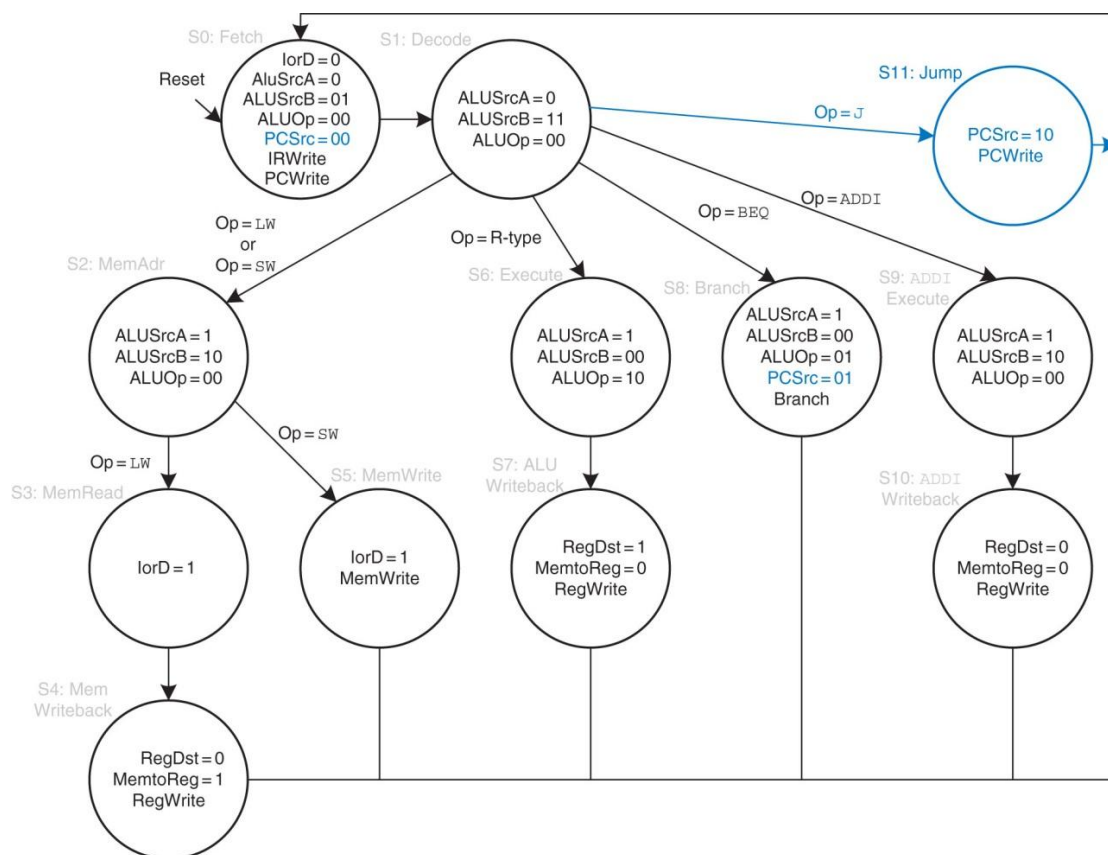

**注意：此图片省略了等待状态，具体参考代码**

在 top 模块中，将各个模块以及线网连接，同时使用多个 assign 或 always 语句将外部组合逻辑电路补全。

另外，在对储存器赋值时，将代码段放置在 0 地址开始，数据段从 0x40 开始（mars 中给出的地址过大，不利于仿真），所以对照代码如下。

20082000 20080100

200d2050 200d0150

8dad0000 8dad0000

200b2054 200b0154

8d6b0000 8d6b0000

200c2054 200c0154

8d8c0004 8d8c0004

ad0b0000 ad0b0000

ad0c0004 ad0c0004

21a9ffff 21a9ffff

8d0b0000 8d0b0000

8d0c0004 8d0c0004

016c5020 016c5020

ad0a0008 ad0a0008

21080004 21080004

2129ffff 2129ffff

1d20fff9 1d20fff9

08000011 08000011

仿真时无输出结果，通过直接查看数据观察结果。

## 五、 意见建议

无。

## 六、 附录

Verilog 实现代码

**top. v**

```
module top(  
    input          clk,  
    input          rst_n,
```



```
output [31:0] dout  
    );
```

```
reg [31:0] pc1;  
reg [31:0] pc;  
wire [31:0] pcjump;  
wire [31:0] adr;  
wire [31:0] rd;  
reg [31:0] instr;  
reg [31:0] data;  
wire      iord;  
wire      memwrite;  
wire      irwrite;  
wire      pcwrite;  
wire      branch;  
wire [1:0] pcsrc;  
wire [2:0] alucontrol;  
wire [1:0] alusrcb;  
wire      alusrca;  
wire      regwrite;  
wire      memtoreg;  
wire      regdst;  
wire [31:0] rd1;
```

```

wire [31:0] rd2;
reg [31:0] a;
reg [31:0] b;
wire [31:0] result;
wire [4:0] writereg;
reg [31:0] signimm;
wire [31:0] signimml2;
wire [31:0] srca;
reg [31:0] srcb;
wire zero;
wire [31:0] alurestult;
reg [31:0] aluout;


always@(posedge clk or posedge rst_n)
begin
    if(rst_n)
        pc <= 32' b0;
    else if(pcen)
        pc <= pc1;
end


assign adr = iord ? aluout : pc;

```

```

always@(posedge clk)
begin
    if(irwrite)
        instr<= rd;
end

always@(posedge clk)
begin
    data <= rd;
end

assign writereg  = regdst ? instr[15:11]
: instr[20:16];

assign result = memtoreg ? data :
aluout;

always@(*)
begin
    if(instr[15])
        signimm = 32'hffff0000 + instr[15:0];
    else
        signimm = 32'h00000000 + instr[15:0];

```

```
end
```

```
assign signimml2[31:2]=  signimm[29:0];
```

```
assign signimml2[1:0]  = 2'h0;
```

```
always@(posedge clk)
```

```
begin
```

```
    a <= rd1;
```

```
end
```

```
always@(posedge clk)
```

```
begin
```

```
    b <= rd2;
```

```
end
```

```
assign srca = alusrca ? a : pc;
```

```
always@(*)
```

```
begin
```

```
    case(alusrcb)
```

```
        2'b00:    srcb = b;
```

```
        2'b01:    srcb = 32'h4;
```

```
        2'b10:    srcb = signimm;
```

```

        2'b11:      srcb = signimm12;
    endcase
end

assign pcjump[31:28]= pc[31:28];
assign pcjump[27:2] = instr[25:0];
assign pcjump[1:0]   = 2'h0;

assign pcen = pcwrite | (branch & zero);

always@(posedge clk)
begin
    aluout <= alurestult;
end

always@(*)
begin
    case(pcsrc)
        2'b00:      pc1  = alurestult;
        2'b01:      pc1  = aluout;
        2'b10:      pc1  = pcjump;
        default:    pc1  = 32'h0;
    endcase

```

```
end
```

```
assign dout          = aluresult;
```

```
control  u_control(  
    .opcode  (instr[31:26]  ),  
    .funct   (instr[5:0]    ),  
    .clk      (clk          ),  
    .rst_n    (rst_n        ),  
    .iord      (iord         ),  
    .memwrite  (memwrite     ),  
    .irwrite   (irwrite      ),  
    .pcwrite   (pcwrite      ),  
    .branch    (branch       ),  
    .pcsrc     (pcsrc        ),  
    .alucontrol (alucontrol[2:0]  ),  
    .alusrcb   (alusrcb[1:0]  ),  
    .alusrca   (alusrca      ),  
    .regwrite  (regwrite     ),  
    .memtoreg  (memtoreg     ),  
    .regdst    (regdst       )  
);
```

```

mem      u_mem(
.clka      (clk      ),
.wea      (memwrite  ),
.addra     (adr[8:2]  ),
.dina      (b[31:0]   ),
.douta     (rd        )
);

```

```

REG_FILE  u_REG_FILE(
.clk       (clk       ),
.r1_addr   (instr[25:21]),
.r2_addr   (instr[20:16]),
.r3_addr   (writereg  ),
.r3_din    (result    ),
.r3_wr     (regwrite  ),
.r1_dout   (rd1       ),
.r2_dout   (rd2       )
);

```

```

alu      u_alu(
.alu_a     (srca      ),
.alu_b     (srcb      ),
.alu_op    (alucontrol),

```

```

        .alu_out      (aluresult    ),
        .alu_zero     (zero         )
    );

```

```

endmodule

```

### **control.v**

```

module control(
    input          [5:0]    opcode,
    input          [5:0]    funct,
    input          clk,
    input          rst_n,
    outputreg      iord,
    outputreg      memwrite,
    outputreg      irwrite,
    outputreg      pcwrite,
    outputreg      branch,
    outputreg      [1:0]    pcsrc,
    outputreg      [2:0]    alucontrol,
    outputreg      [1:0]    alusrcb,
    outputreg      alusrca,
    outputreg      regwrite,
    outputreg      memtoreg,

```



```
outputreg          regdst
    );
```

```
reg [3:0] curr_state;
reg [3:0] next_state;
```

```
always@(posedge clk or posedge rst_n)
begin
    if(rst_n)
        curr_state <= 4'h0;
    else
        curr_state <= next_state;
end
```

```
always@(*)
begin
    case(curr_state)
        4'd0: next_state = 4'd1;
        4'd1: begin
            case(opcode)
                6'b100011: next_state = 4'd2;
                6'b101011: next_state = 4'd2;
                6'b000000: next_state = 4'd6;
```

```

        6' b000111: next_state = 4' d8;
        6' b001000: next_state = 4' d9;
        6' b000010: next_state = 4' d11;
        default:   next_state = 4' d0;
    endcase
end
4' d2: begin
    case(opcode)
        6' b100011: next_state = 4' d3;
        6' b101011: next_state = 4' d5;
        default:   next_state = 4' d0;
    endcase
end
4' d3: next_state = 4' d12;
4' d4: next_state = 4' d0;
4' d5: next_state = 4' d14;
4' d6: next_state = 4' d7;
4' d7: next_state = 4' d0;
4' d8: next_state = 4' d15;
4' d9: next_state = 4' d10;
4' d10: next_state = 4' d0;
4' d11: next_state = 4' d15;
4' d12: next_state = 4' d4;

```

```

        4' d13:  next_state =  4' d14;
        4' d14:  next_state =  4' d15;
        4' d15:  next_state =  4' d0;
        default:  next_state =  4' d0;
    endcase
end

always@(*)
begin
    case(curr_state)
        4' d0:begin
            iord=1' b0;
            memwrite=1' b0;
            irwrite=1' b1;
            pcwrite=1' b1;
            branch=1' b0;
            pcsrc=2' b0;
            alucontrol=3' b001;
            alusrcb=2' b01;
            alusrca=1' b0;
            regwrite=1' b0;
            memtoreg=1' b0;
            regdst=1' b0;

```

```

        end
4' d1: begin
        iord=1' b0;
        memwrite=1' b0;
        irwrite=1' b0;
        pcwrite=1' b0;
        branch=1' b0;
        pcsrc=2' b0;
        alucontrol=3' b001;
        alusrcb=2' b11;
        alusrca=1' b0;
        regwrite=1' b0;
        memtoreg=1' b0;
        regdst=1' b0;
    end
4' d2: begin
        iord=1' b0;
        memwrite=1' b0;
        irwrite=1' b0;
        pcwrite=1' b0;
        branch=1' b0;
        pcsrc=2' b0;
        alucontrol=3' b001;

```

```

        alusrcb=2'b10;
        alusrca=1'b1;
        regwrite=1'b0;
        memtoreg=1'b0;
        regdst=1'b0;
    end
4'd3:begin
        iord=1'b1;
        memwrite=1'b0;
        irwrite=1'b0;
        pcwrite=1'b0;
        branch=1'b0;
        pcsrc=2'b0;
        alucontrol=3'b001;
        alusrcb=2'b0;
        alusrca=1'b0;
        regwrite=1'b0;
        memtoreg=1'b0;
        regdst=1'b0;
    end
4'd4:begin
        iord=1'b0;
        memwrite=1'b0;

```

```
irwrite=1'b0;
pcwrite=1'b0;
branch=1'b0;
pcsrc=2'b0;
alucontrol=3'b001;
alusrcb=2'b0;
alusrca=1'b0;
regwrite=1'b1;
memtoreg=1'b1;
regdst=1'b0;
```

```
end
```

```
4'd5:begin
```

```
iord=1'b1;
memwrite=1'b1;
irwrite=1'b0;
pcwrite=1'b0;
branch=1'b0;
pcsrc=2'b0;
alucontrol=3'b001;
alusrcb=2'b0;
alusrca=1'b0;
regwrite=1'b0;
memtoreg=1'b0;
```

```

        regdst=1'b0;
    end
4'd6:begin
    iord=1'b0;
    memwrite=1'b0;
    irwrite=1'b0;
    pcwrite=1'b0;
    branch=1'b0;
    pcsrc=2'b0;
    alucontrol=3'b001;
    alusrcb=2'b0;
    alusrca=1'b1;
    regwrite=1'b0;
    memtoreg=1'b0;
    regdst=1'b0;
end
4'd7:begin
    iord=1'b0;
    memwrite=1'b0;
    irwrite=1'b0;
    pcwrite=1'b0;
    branch=1'b0;
    pcsrc=2'b0;

```

```

        alucontrol=3'b001;
        alusrcb=2'b0;
        alusrca=1'b0;
        regwrite=1'b1;
        memtoreg=1'b0;
        regdst=1'b1;
    end
4'd8:begin
        iord=1'b0;
        memwrite=1'b0;
        irwrite=1'b0;
        pcwrite=1'b0;
        branch=1'b1;
        pcsrc=2'b1;
        alucontrol=3'b100;
        alusrcb=2'b0;
        alusrca=1'b1;
        regwrite=1'b0;
        memtoreg=1'b0;
        regdst=1'b0;
    end
4'd9:begin
        iord=1'b0;

```



```

        memwrite=1'b0;
        irwrite=1'b0;
        pcwrite=1'b0;
        branch=1'b0;
        pcsrc=2'b0;
        alucontrol=3'b001;
        alusrcb=2'b10;
        alusrca=1'b1;
        regwrite=1'b0;
        memtoreg=1'b0;
        regdst=1'b0;
    end

4'd10:  begin
        iord=1'b0;
        memwrite=1'b0;
        irwrite=1'b0;
        pcwrite=1'b0;
        branch=1'b0;
        pcsrc=2'b0;
        alucontrol=3'b001;
        alusrcb=2'b0;
        alusrca=1'b0;
        regwrite=1'b1;

```

```

        memtoreg=1'b0;
        regdst=1'b0;
    end
4'd11:  begin
        iord=1'b0;
        memwrite=1'b0;
        irwrite=1'b0;
        pcwrite=1'b1;
        branch=1'b0;
        pcsrc=2'b10;
        alucontrol=3'b001;
        alusrcb=2'b0;
        alusrca=1'b0;
        regwrite=1'b0;
        memtoreg=1'b0;
        regdst=1'b0;
    end
default:  begin
        iord=1'b0;
        memwrite=1'b0;
        irwrite=1'b0;
        pcwrite=1'b0;
        branch=1'b0;

```

```

        pcsrc=2'b10;
        alucontrol=3'b0;
        alusrcb=2'b0;
        alusrca=1'b0;
        regwrite=1'b0;
        memtoreg=1'b0;
        regdst=1'b0;
    end

endcase

end

endmodule

```

### **REG\_FILE. v**

```

module REG_FILE(
    input                clk,
    input                [4:0]  r1_addr,
    input                [4:0]  r2_addr,
    input                [4:0]  r3_addr,
    input                [31:0]  r3_din,
    input                r3_wr,
    outputreg            [31:0]  r1_dout,
    outputreg            [31:0]  r2_dout

```

```
);
```

```
reg [31:0] data [31:0];
```

```
always@(posedge clk)
```

```
begin
```

```
    if(r3_wr)
```

```
        data[r3_addr] <= r3_din;
```

```
end
```

```
always@(*)
```

```
begin
```

```
    if(r1_addr)
```

```
        r1_dout = data[r1_addr];
```

```
    else
```

```
        r1_dout = 32'h0;
```

```
end
```

```
always@(*)
```

```
begin
```

```
    if(r2_addr)
```

```
        r2_dout = data[r2_addr];
```

```
    else
        r2_dout = 32'h0;
    end
```

```
endmodule
```

### **alu.v**

```
module alu(
    input signed [31:0] alu_a,
    input signed [31:0] alu_b,
    input      [2:0] alu_op,
    outputreg [31:0] alu_out,
    outputreg          alu_bgtz
);

always@(*)
begin
    case(alu_op)
        3'h00:    alu_out = 32'h0;
        3'h01:    alu_out = alu_a + alu_b;
        3'h02:    alu_out = alu_a - alu_b;
        3'h03:    alu_out = alu_a & alu_b;
        3'h04:    alu_out = alu_a | alu_b;
```

```

        3'h05:    alu_out = alu_a ^ alu_b;
        3'h06:    alu_out = ~(alu_a | alu_b);
        default:    alu_out = 32'h0;

    endcase

end

always@(*) //for bgtz
begin
    if(alu_out <= 0)
        alu_bgtz    = 1'h0;
    else
        alu_bgtz    = 1'h1;
    end

end

endmodule

```

### **mem. coe**

```

memory_initialization_radix = 16;
memory_initialization_vector = 20080100
200d0150
8dad0000
200b0154
8d6b0000

```

200c0154

8d8c0004

ad0b0000

ad0c0004

21a9fffe

8d0b0000

8d0c0004

016c5020

ad0a0008

21080004

2129ffff

1d20fff9

08000011

00000000

00000000

00000000

00000000

00000014

00000003

00000003


00000000;

mem

Block Memory Generator

Documents View

IP Symbol

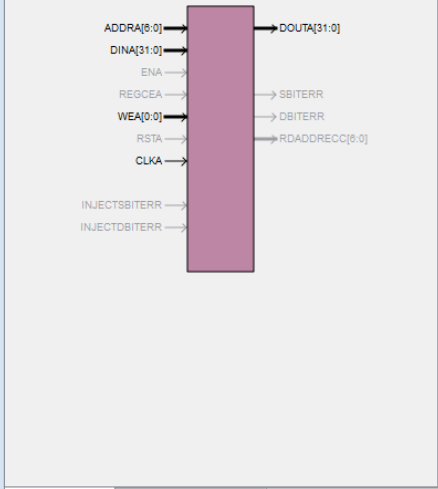

LogiCORE **Block Memory Generator** 4.3

Component Name: mem

Memory Type: Single Port RAM

Clocking Options

☐ Common Clock

ECC Options

ECC Type: No ECC

☐ Use Error Injection Pins: Single Bit Error Injection

Write Enable

☐ Use Byte Write Enable

Byte Size: 9 bits

Algorithm

Defines the algorithm used to concatenate the block RAM primitives. See the datasheet for more information.

☒ Minimum Area

☐ Low Power

☐ Fixed Primitives

Primitive (Write Port A): 8x2

Actual Primitive(s) Used: 4x2, 8x2


IP Symbol Power Estimation

Datasheet < Back Page 1 of 5 Next > Generate Cancel Help

Block Memory Generator

Documents View

IP Symbol

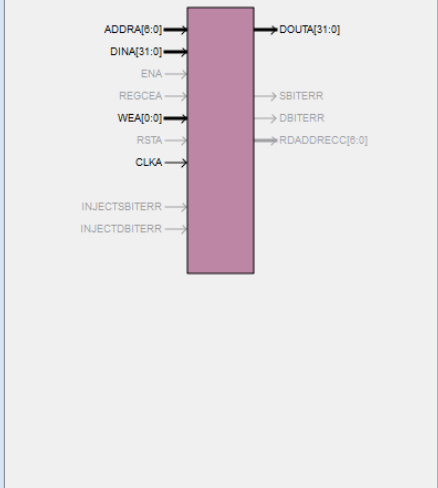

LogiCORE **Block Memory Generator** 4.3

Port A Options

Memory Size

Write Width: 32 Range: 1..1152 Read Width: 32

Write Depth: 128 Range: 2..9011200 Read Depth: 128

Operating Mode

☒ Write First

☐ Read First

☐ No Change



Enable

☒ Always Enabled

☐ Use ENA Pin

IP Symbol Power Estimation

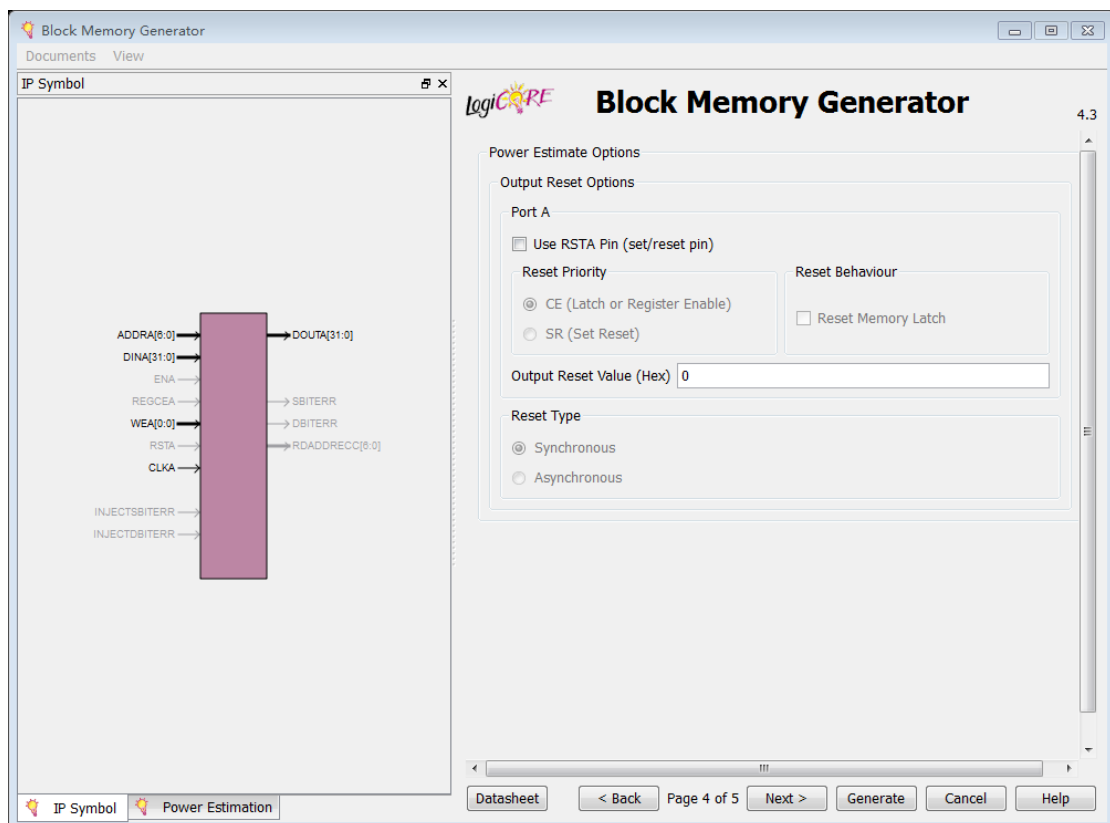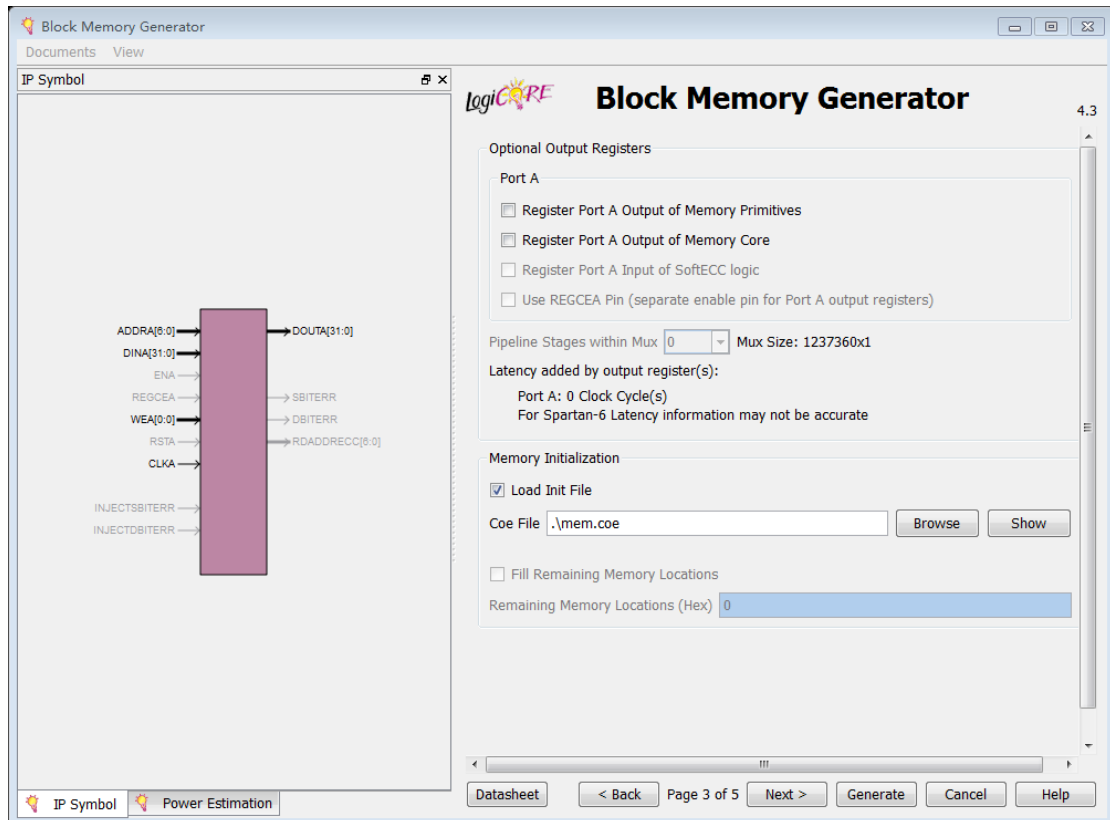
Datasheet < Back Page 2 of 5 Next > Generate Cancel Help




Block Memory Generator

DocumentsView

IP Symbol

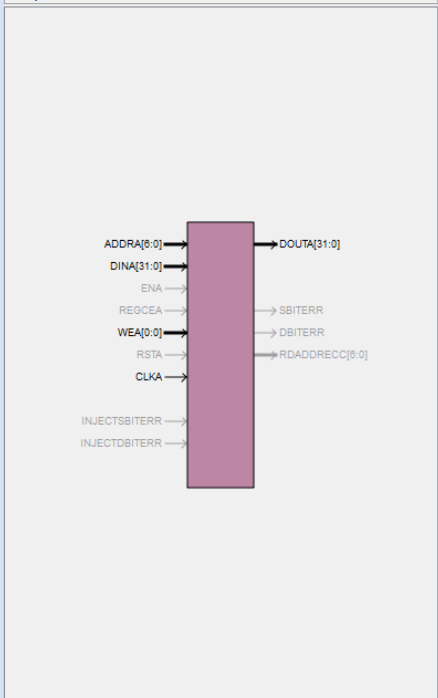

The diagram shows a central purple rectangular block representing the memory core. On the left side, there are input ports: ADDR[8:0], DINA[31:0], ENA, REGCEA, WEA[0:0], RSTA, CLKA, INJECTSBITERR, and INJECTDBITERR. On the right side, there are output ports: DOUTA[31:0], SBITERR, DBITERR, and RDADRECC[8:0].

 **Block Memory Generator** 4.3

Structural/Unisim Simulation Model Options

Defines the type of warnings and outputs are generated when a read-write or write-write collision occurs.

☒ All  
☐ None  
☐ Warning Only  
☐ Generate X-Only

Behavioral Simulation Model Options

☐ Disable Collision Warnings  
☐ Disable Out of Range Warnings

Information

Memory Type: Single Port Memory  
Block RAM resource(s) (9K BRAMs): 1  
Block RAM resource(s) (18K BRAMs): 0  
Total Port A Read Latency (From Rising Edge of Read Clock): 1 Clock Cycle(s)  
Address Width A: 7  
The Block Memory Generator core is not fully backward compatible with the Single Port and Dual Port Block Memory cores. Please see the datasheet for more information.

IP SymbolPower Estimation

Datasheet< BackPage 5 of 5Next >GenerateCancelHelp